

# Common Emitter with $R_E$ that is partially bypassed by $C_E$ .

## Richard Cooper

$V_{out}$  is inverted so the gain  $A_v$  and  $A_i$  are negative.

$R_E = R_{ef} + R_{eb}$  the total  $R_E$  for the DC bias design.

$R_{ef}$  is the portion of  $R_E$  that is not bypassed by  $C_E$ .

$R_{eb}$  is the portion of  $R_E$  that is bypassed by  $C_E$ .

The first step is to find the Transistor characteristics around the estimated Q-point

1. Choose  $V_E$ : Step CEwRef 1.1

2. Estimate the  $I_C$  collector current Qpoint: Step CEwRef 1.2: Choose  $I_C$  est, only used the VI curves.

3. The saturated  $V_{ce}$  voltage  $V_{CE-sat}$ : Step CEwRef 1.3:

4. Calculate the midpoint  $V_C$ : Step CEwRef 1.4:

5. Find  $r_o$ ,  $\beta_{AC}$ ,  $V_{ceSAT}$ , and  $r_{\pi}$ : Step CEwRef 1.5

$r_o = \Delta V_{CE} / \Delta I_C$  the slope of a line thru Q-point.

$\beta_{AC} = \Delta I_C / \Delta I_B$  measured around Q-point est.

$\beta_{DC} = I_C / I_B$  measured around Q-point est

$V_{ceSAT} = V_{ce}$  begins to flatten.

$r_{\pi} = (\beta V_T) / I_C$   $r_{\pi}$  is base to emitter resistance of the Hybrid Pie model.


Where  $V_T = kT/q$  at room temperature is  $V_T \approx 26mV$ .

Plot the estimated Q-point ( $V_{CE}, I_C$ ) on the BJT characteristics curve.

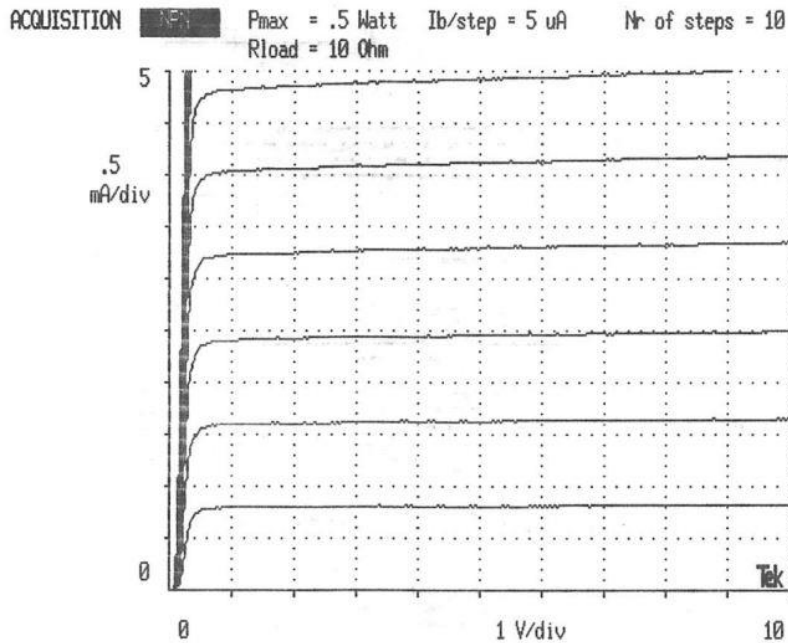**Note: If the equation has Just  $\beta$  the use  $\beta_{AC}$ .**

Skip to CEwRef Part 2: if you are given are  $V_{ceSAT}$ ,  $r_o$ ,  $r_{\pi}$  and  $\beta$ .

CEwRef Part 1: Measure the device parameters  $V_{CE_{SAT}}$ ,  $r_o$ ,  $r_{\pi}$  and  $\beta$  from the VI curves of the transistor (BJT).



**Characteristics Curve 2N3904 First Ib curve Ib = 5uA**

**X axis is  $V_{CE}$ , Y axis is  $I_C$**


To find which  $I_B$  curve you are you on count from a known cure (First  $I_B$  curve  $I_B = 5\mu A$ ) by the step size at the top of the curve label step =  $5\mu A$ .

**$r_o = \Delta V_{CE} / \Delta I_C$**  Where  $V_{CE}$  is the X Axis. We do not want to start at zero because the first part of the curve is nonlinear we want to use the area where the curve is liner. So chose  $V_{CE}$  between  $1V$  to  $10V = 10V \Delta V_{CE} = 10V - 1V = 9V$ . Where  $I_C$  is the Y Axis. We pick an  $I_B$  curve close to out estimated or actual Q-Point and measure the current  $I_C$  at two points along the  $I_B$  curve at  $V_{CE} = 1V$  the second  $I_C$  current at  $V_{CE} = 10V \Delta I_C = 7.3mA - 7.0mA = 0.3mA$  The calculation of  $r_o$  at the chosen  $I_B$  curve  **$r_o = \Delta V_{CE} / \Delta I_C = 9V / 0.3mA = 30k\Omega$** .

**$B_{AC} = \Delta I_C / \Delta I_B$**  at the  $V_{CE}$  (from step **CEwRef 2.2:**) on the X-Axis find the  $\Delta I_B$  which is the current  $I_B$  between the two  $I_B$  cures on both sides of the Q-Point. Where the 2  $I_C$  the currents associated with the 2 points on the  $I_B$  curves at  $V_{CE}$ .

**$\beta_{DC} = I_C / I_B$**  at the  $V_{CE}$  (from step **CEwRef 2.2:**) on the X-Axis find the  $I_B$  which is the current  $I_B$  form the cures closes to the Q-Point. Where the  $I_C$  the currents associated with the point on the  $I_B$  curves at  $V_{CE}$ .

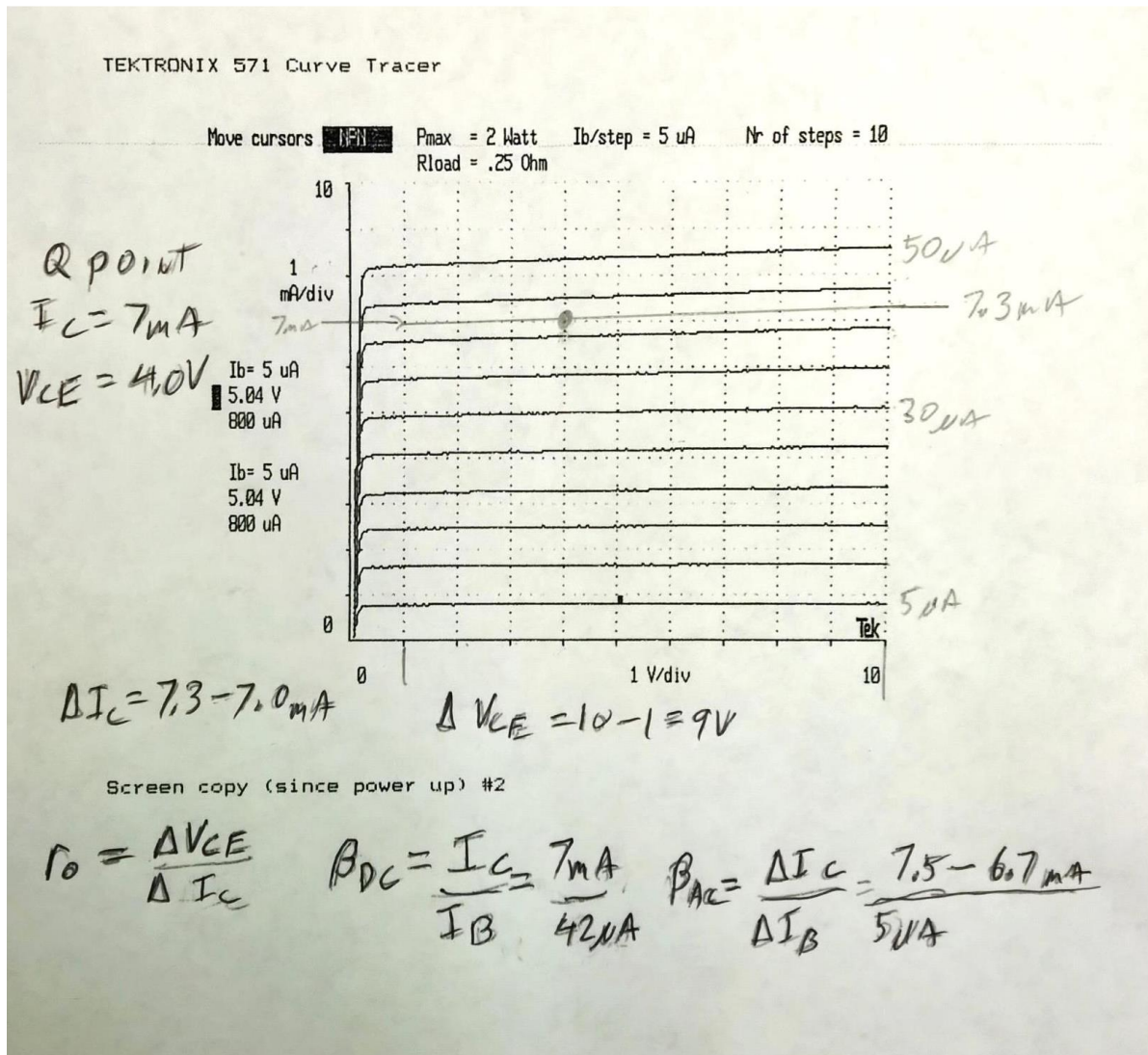Note: If the equation has Just  $\beta$  the use  $B_{AC}$ .



Characteristics Curve for 2N2222

Sample calculation not your solution.

For the design of the amplifier, the 4 parameter values required are  $V_{CE_{SAT}}$ ,  $r_o$ ,  $r_{\pi}$  and  $\beta$ . Derived from the transistor characteristics curve shown in BJT above, one can set an approximate Q-point ( $V_{CE}$  and  $I_C$ ) in the active region and measure  $r_o$  and  $\beta$ . We will solve for  $V_{ce}$  and estimate  $I_c$ .

### Step CEwRef 1.1: Choose $V_{Re}$ Same as Step CEwRef 2.1

Because  $V_{BE}$  will decrease  $\approx 2.5\text{mV} / ^\circ\text{C}$  rise we set  $V_E =$  between 2V to 3V.  $V_E$  and  $R_E$  will provide negative feedback to stabilize  $\beta$  and  $V_{BE}$ .

### Step CEwRef 1.2: Choose $I_C$ estimate.

For an approximate  $I_C$  Q-point use  $I_C \approx 3.0 * I_{load}$  peak this is not the solution to your design  $I_C$  Q-point. We can use an approximate  $I_C$  because  $r_o$  and  $\beta$  will not change very much with small changes in Q-point.

### Step CEwRef 1.3: $V_{ceSAT}$ (Vce saturation voltage)

The  $V_{ceSAT}$  (Vce saturation voltage) are found from the BJT characteristics curve where the curve begins to flatten out  $\approx 0.2$  Vdc.

### Step CEwRef 1.4: Calculate the midpoint $V_C$

Re partially bypassed  $R_e = R_{eb} + R_{ef}$

Same as **Step CEwRef 2.2**

Midpoint selection will allow for maximum output voltage swing.

We will add 20% to  $V_{out}$  so the design is not on the edge of the solution. This will also help with the additional loading because of high frequency capacitors as the frequency approaches the high frequency break points.

$$V_{C(max)} = V_{CC} - (V_{out} + 20\%V_{out})$$

$$V_{C(min)} = V_E + V_{CE\ sat} + (V_{out} + 20\%V_{out})$$

$$V_C = (V_{C(max)} + V_{C(min)}) / 2 \quad \text{Midpoint } V_C \text{ Q-point}$$

$$V_{CE} = V_C - V_E \quad \text{This is the Q-point } V_{CE}$$

$$V_E = V_{Re} - V_{ee}$$

### Step CEwRef 1.5 find $r_o$ , $\beta_{AC}$ , $V_{ceSAT}$ , and $r_{\pi}$ .

$r_o = \Delta V_{CE} / \Delta I_C$  the slope of a line thru Q-point collector to emitter resistance of Hybrid Pie model.

$\beta_{AC} = \Delta I_C / \Delta I_B$  measured around Q-point est.

$V_{ceSAT} =$  the Vce where the VI curve begins to flatten.

$r_{\pi} = (\beta V_T) / I_C$   $r_{\pi}$  is base to emitter resistance of Hybrid Pie model.

Where  $V_T = kT/q$  at room temperature is  $V_T \approx 26\text{mV}$ .

Plot the estimated Q-point ( $V_{CE}, I_C$ ) on the BJT characteristics curve.

## CEwRef Part 2: selecting Rc, RE = Ref +Reb , Ic and IE.

Using BJT parameters and Vcc, Vout, and Rload, Rin

### Step CEwRef 2.1: Choose VRe

Because  $V_{BE}$  will decrease  $\approx 2.5\text{mV} / ^\circ\text{C}$  rise we set  $V_{Re} =$  between 2V to 3V.  $V_{Re}$  and  $R_E$  will provide negative feedback to stabilize  $\beta$  and  $V_{BE}$ .

### Step CEwRef 2.2: Calculate the midpoint Vc

Re partially bypassed  $R_e = R_{eb} + R_{ef}$

Midpoint selection will allow for maximum output voltage swing.

We will add 20% to Vout so the design is not on the edge of the solution. This will also help with the additional loading because of high frequency capacitors as the frequency approaches the high frequency break points.

$$V_{C(max)} = V_{CC} - (V_{out} + 20\%V_{out})$$

$$V_{C(min)} = V_E + V_{CE\text{ sat}} + (V_{out} + 20\%V_{out})$$

$$V_C = (V_{C(max)} + V_{C(min)}) / 2 \quad \text{Midpoint } V_C \text{ Q-point}$$

$$V_{CE} = V_C - V_E \quad \text{This is the Q-point } V_{CE}$$

### Step CEwRef 2.3: Calculate Rc .

Looking into the collector we see  $r_o + R_{ef} \parallel [ (r_{\pi} + R_{b1} \parallel R_{b2} \parallel (R_i + R_{gen})) ] / (\beta + 1) \approx r_o$  so we will use just  $r_o$ .

The DC equation:  $V_{RC} = V_{CC} - V_C = I_C R_C$  voltage across Rc derived from Vcc and Q-point Vc.

The AC equation:  $V_{outP} = i_c ( R_C \parallel r_o \parallel R_L )$  output voltage  $V_{out_{peak}}$

Rewrite AC:  $V_{out} = I_C R_C ( r_o \parallel R_L ) / ( R_C + ( r_o \parallel R_L ) )$  Parallel resistance equation

Substituting in  $V_{RC} = I_C R_C$

Combined equation:  $V_{out} = V_{RC} ( r_o \parallel R_L ) / ( R_C + ( r_o \parallel R_L ) )$

Solve for Rc; Add 20%Vout so the collector current is not set to an edge.

$$R_C = \frac{V_{CC} - V_C}{V_{out} + 20\%V_{out}} ( r_o \parallel R_L ) - ( r_o \parallel R_L )$$

**Step CEwRef 2.4: Calculate  $I_C$ ,  $I_E$ , and  $R_e$ .**

These are not the estimate values from Part 1

$I_C = (V_{CC} - V_C) / R_C$  The Q-point collector current.


$I_B = I_C / \beta_{DC}$  The base current.

$I_E = I_C (\beta_{DC} + 1) / \beta_{DC}$  emitter current.


$R_e = V_{Re} / I_E = (V_e + V_{ee}) / I_E$  Total emitter resistance.

Thus, Q-point is  $(V_{CE}, I_C)$ .

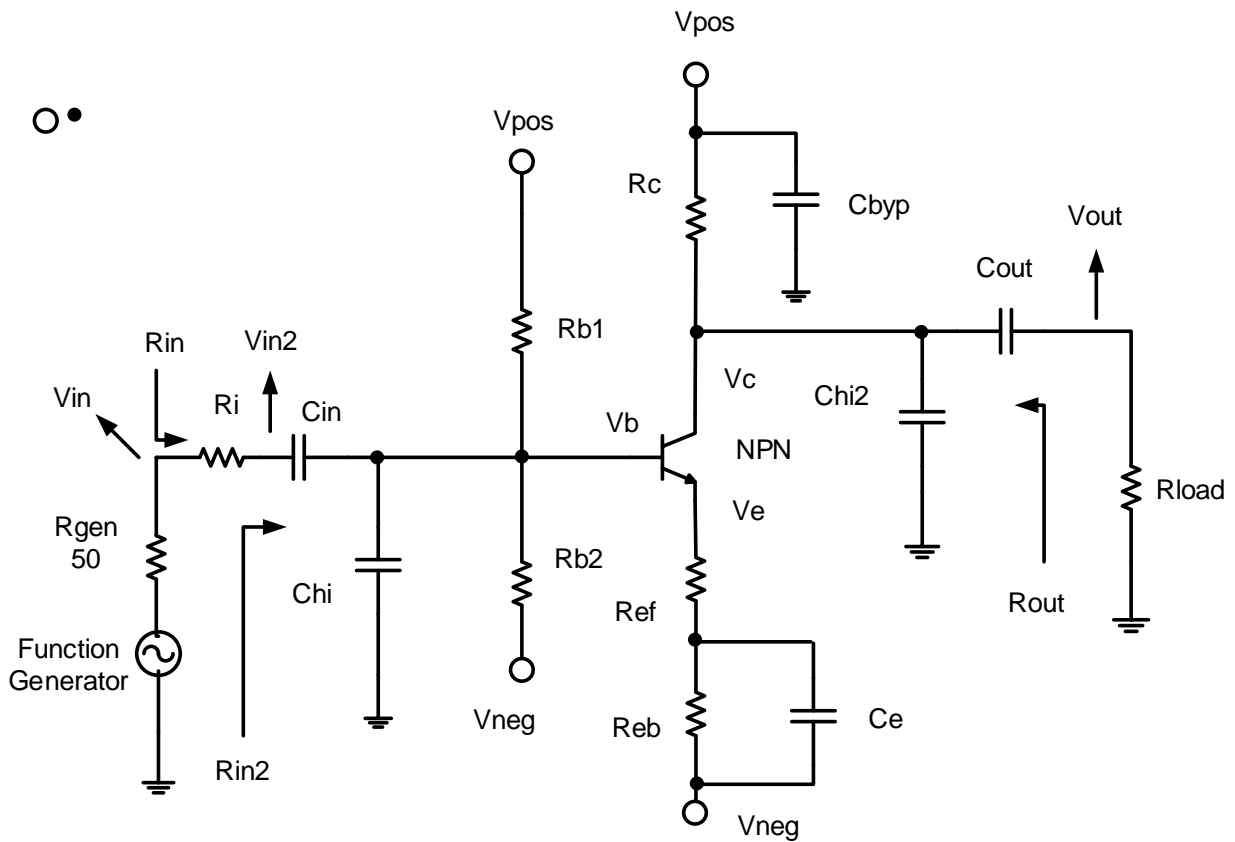We now have,  $V_E, V_C, R_C, R_e, I_C, I_E, V_{CE}, V_{CEsat}$



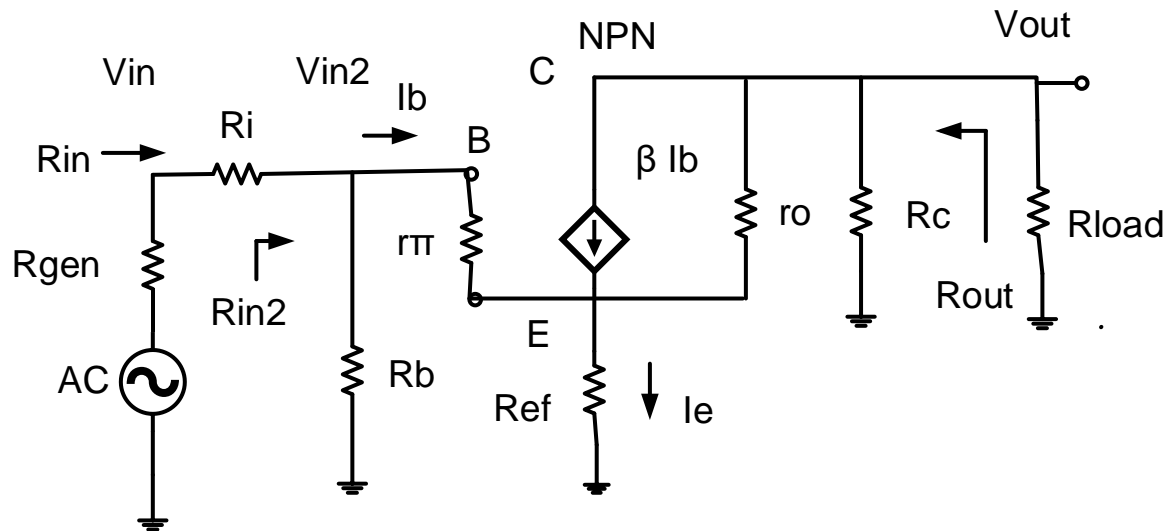**CEwRef Figure 1: Amplifier with emitter partially bypassed.**



**CEwRef Figure 2: Small signal model with partial bypass of Re**

**CEwRef Part 3 Calculating impedance and Gain with Ref use Figure 2.**

Remember the gain  $A_v$  and  $A_i$  are negative for a common emitter amplifier.

We use the same Q-point and bias resistors  $R_{b1}$ ,  $R_{b2}$ ,  $R_c$ , and  $R_e = R_{ref} + R_{eb}$ .

**Step CEwRef 3.1: Find Ref based on Voltage Gain requested**

Note:  $i_b$  is the AC base current that results from  $V_{in}$ .

Looking into the collector we see  $r_o + R_{ref} \parallel [ (r_{\pi} + R_{b1} \parallel R_{b2} \parallel (R_i + R_{gen}) ) / (\beta + 1)$

Because the term  $( (R_i + R_{gen}) \parallel R_b ) + r_{\pi} / (\beta + 1)$  is small and it is in parallel with  $R_{ref}$  at the emitter therefore we will use  $r_o$  for the approximation.

AC voltage  $V_{out} = -\beta i_b (R_c \parallel R_{load} \parallel r_o)$  Note: use the approximat  $r_o$  because  $R_{ref}$  is not known yet.

We do not need to solve for the AC signal  $i_b$  because it will be cancelled out later.

AC voltage  $V_{in} = (R_{in}/R_{in2}) V_{in2}$  Input signal from the function generator.

AC voltage  $V_{in2} = i_b (r_{\pi} + (\beta + 1) R_{ref})$  Input signal on the base

Given  $R_{in}$  calculate  $R_{in2}$ .

$R_{in2} = R_{in} - R_i$  Solve  $R_{in2}$  needed to meet the  $R_{in}$  requirements.

$A_{v2} = A_v * R_{in} / R_{in2}$   $A_{v2}$  at base is the gain needed to meet  $A_v$  requested. For CE  $A_v$  is negative.

$A_{v2} = V_{out} / V_{in2} = -\beta (R_c \parallel r_o \parallel R_{load}) / (r_{\pi} + (\beta + 1) R_{ref})$  voltage gain at base, we do not need to find  $i_b$  since  $i_b$  cancels.  $A_{v2}$  is negative which means that  $V_{out}$  is inverted.

### Step CEwRef 3.2: Solve for Ref by using gain at base Av2.

$Ref = [ (-\beta (Rc \parallel ro \parallel Rload) / Av2) - r\pi ] / (\beta + 1)$  from Av2 or use equation below

### Step CEwRef 3.3: Solve for Ref by using overall gain Av.

$$Av = Av2 * Rin2 / Rin$$

$$Av = Vout / Vin = -\beta (Rc \parallel ro \parallel Rload) / (Rin/Rin2) (r\pi + (\beta + 1) Ref)$$
 voltage gain at input

We can see that voltage gain Av can be controlled by the value of Ref

$$Av = -\beta (Rin2/Rin) (Rc \parallel ro \parallel Rload) / (r\pi + (\beta + 1) Ref)$$

Rearrange Av to solve for Ref from requested Av. Where Av is overall gain,

$$Ref = \{[-\beta (Rin2/Rin) (Rc \parallel ro \parallel Rload) / Av] - r\pi\} / (\beta + 1)$$

Remember Av is negative

Step CEwRef 3.4: Solve for Reb from Re and Ref

Remember that Re is the total emitter resistance from step CEwRef 2.4.

$$Reb = Re - Ref$$

### CEwRef Part 4: Find Rb1, Rb2, Rin, Rout, Ai, Power Gain G, Vin, and Voc of function generator.

#### Step CEwRef 4.1: Find Rb1 and Rb2 based on requested Rin

Require Rin set to a given value. Need Vcc, Vb, rπ and IB (DC bias base current).  
Given Rin calculate Rin2.

$$Rin2 = Rin - Ri \quad \text{Solve Rin2 needed to meet the Rin requirements.}$$

Solve for Rb from Rin2 and Rbase.

$$Rbase = r\pi + (\beta_{DC} + 1) (Ref \parallel (ro + Rc \parallel Rload)) \quad \text{Looking into the Base of the BJT.}$$

$$Rb = 1 / ((1 / Rin2) - (1 / Rbase)) \quad \text{Solve for Rb needed to Rin requirements.}$$

Find Rb1 first then Rb2

$$IB = IC / \beta_{DC} \quad \text{DC bias base current.}$$

$$Rb1 = (Vcc - Vee) / (((Vb - Vee) / Rb) + IB) \quad \text{Solve for Rb1.}$$

$$IRb1 = Vcc - VB / Rb1 \quad \text{Current thru Rb1}$$

$$IRb2 = IRb1 - IB \quad \text{Current thru Rb2. Solve Rb2 from VB - Vee and current thru Rb2:}$$

$$Rb2 = (VB - Vee) / IRb2 = VB / (((Vcc - VB) / Rb1) - IB)$$

#### Step CEwRef 4.2: Input Impedance: AC characteristics

$$Rb = Rb1 \parallel Rb2$$

Where Ref is the part of Re that is not bypassed by CE.

$$Rbase = r\pi + (\beta + 1) (Ref \parallel (ro + Rc \parallel Rload)) \quad \text{Looking into the Base of the BJT.}$$

$$Rin2 = Rb \parallel Rbase$$

$$Rin = Ri + Rin2$$



### Step CEwRef 4.3: Output Impedance Rout with Ref

If Re partially bypassed with CE bypassing Ref.

$$R_b = R_{b1} \parallel R_{b2}$$

RemitterBase is the impedance looking in the BJT emitter toward the base.

$$\text{RemitterBase} = (r_{\pi} + R_b \parallel (R_i + R_{gen})) / (\beta + 1) \quad \text{Small value, because divided by } \beta + 1.$$

The complete equation below for Rout,

$$R_{out} = R_c \parallel (r_o + R_{ref} \parallel [r_{\pi} + R_b \parallel (R_i + R_{gen})] / (\beta + 1))$$

Because ro is greater than 30kΩ.

You text book may approximate  $R_{out} = R_c \parallel \text{"large"} = R_c$ .

### Step CEwRef 4.4: Current Gain Ai

The current gain Ai can be obtained  $i_{load}$  and  $i_{in}$  or calculated from Av Rin and Rload.

$$A_i = \frac{i_{load}}{i_{in}} = \frac{v_{out}/R_{load}}{v_{in}/R_{in}} = A_v \frac{R_{in}}{R_{load}}$$

### Step CEwRef 4.5: Power gain G

$$G = P_{out} / P_{in} = V_{out} * I_{load} / V_{in} * I_{in} = A_v * A_i$$

$$\text{In decibels } G_{dB} = 10 \log ( A_v * A_i )$$

### Step CEwRef 4.6: Vin and Voc of Vgen

Input signal level need to produce the required output voltage.

$$V_{in} = V_{out} / A_v$$

The open circuit voltage of the generator to produce the required output voltage.

Because of the Voltage divider between Vgen and Vin. The output impedance of the function generator is Rgen = 50Ω and the input impedance Rin of the amplifier. Voc is the setting of the voltage set on the function generator.

$$V_{oc} \text{ of } V_{gen} = V_{in} (R_{gen} + R_{in}) / R_{in} \quad V_{gen} \text{ is larger than } V_{in}$$

Use this value in LTspice and the laboratory Function generator for output of signal source.

## CEwRef Part 5: Frequency response with Ref

With the Q-point being set after the sequence of steps, we can go for the selection of capacitors and finally connect the signal generator at input and measure the output waveform.

### Step CEwRef 5.1: Low frequency cut off. $F_L$

First we will select  $C_{in}$ ,  $C_{out}$  and  $C_E$  which jointly would set the roll-off beyond the lower cut-off frequency. Set any frequency within the range as your lower cut-off frequency and let us call it  $f_L$ . Three capacitors will introduce 3 zeros in the transfer function of the system. Because we will set 3 zeros at the same frequency we must use the Band Width Shrinkage factor.

$$BW_{shrinkage} = \sqrt{2^{\frac{1}{n}} - 1}$$

Where n is the number of zeros for low frequency breakpoints at same frequency.

The low frequency cutoff average of the individual time constants with shrinkage factor applied be we have set all the time constants the same.

$$f_L = \frac{f_{C_{in}} + f_{C_{out}} + f_{C_E}}{3\sqrt{2^{\frac{1}{3}} - 1}}$$

### Setting 3 frequencies equal, we get,

$$f_{C_{in}} = f_{C_{out}} = f_{C_E} = f_L \sqrt{2^{1/3} - 1}$$

Find the C for each breakpoint  $f_{C_{in}}$ ,  $f_{C_{out}}$ , and  $f_{C_E}$  where  $n = 3$ .

$$C = \frac{1}{2\pi f_c (R \text{ seen by } C)}$$

Where C is the capacitor that sets the breakpoint  $f_c$

R is the Thevenin equivalent resistance seen by the capacitor.

RemitterBase is the impedance looking in the BJT emitter to base.

RemitterbBase =  $(r_{\pi} + R_b \parallel (R_i + R_{gen})) / (\beta + 1)$  Small value

$R_{CE} = R_{eb} \parallel (R_{ef} + (r_o + R_C \parallel R_{Load}) \parallel \text{RemitterBase})$

### Step CEwRef 5.2: High frequency cut off. $F_H$

$C_{hi}$  Sets the higher cut-off frequency  $f_H$  which is to be set from the specified range.

In this case because  $C_{hi}$  and  $C_{hi2}$  are to the same break point. We must use the band shrinkage factor with  $n = 2$ . We need only to find a two poles at  $F_H / \text{bandshrinkage} = f_{chi} = f_{ch2}$  to set the high frequency cutoff.

$$\text{Set } F_{chi} = F_{chi2} = F_H / \sqrt{2^{1/2} - 1}$$

$$R_b = R_{b1} \parallel R_{b2} \quad \text{Base bias resistors}$$

$$R_{base} = r_{\pi} + (\beta + 1) (R_{ef} \parallel (r_o + R_c \parallel R_{load})) \quad \text{Looking into the Base of the BJT.}$$

$$R_{in2} = R_b \parallel R_{base}$$

$$R \text{ seen by } C_{hi} \quad R_{Chi} = (R_{gen} + R_i) \parallel R_{in2}$$

$$C_{hi} = \frac{1}{2\pi f_{Chi} (R \text{ seen by } C_{hi})}$$

$$R \text{ seen by } C_{hi2} \quad R_{Chi2} = R_{out} \parallel R_{load} \quad \text{Note: use the correct } R_{out} \text{ depending on } R_{ef}$$

$$C_{hi2} = \frac{1}{2\pi f_{Chi2} (R \text{ seen by } C_{hi2})}$$

The following table list the equivalent resistance expressions seen by the capacitors.

Capacitor	Resistance seen by Capacitor
RemitterBase	$(r_{\pi} + R_b \parallel (R_i + R_{gen})) / (\beta + 1)$
$C_{in}$	$R_{gen} + R_i + R_{in2}$
$C_{out}$	$R_{Load} + R_{out}$
$C_E$	$R_{eb} \parallel (R_{ef} + (r_o + R_c \parallel R_{Load}) \parallel R_{emitterBase})$
$C_{hi}$	$(R_{gen} + R_i) \parallel R_{in2}$
$C_{hi2}$	$R_{out} \parallel R_{load}$

**CEwRef Table 1: Resistance Seen By Capacitors**