

FOR BIAS $R_E = R_{E1} + R_{E2}$

Given

V_{OUT_PEAK} , R_{LOAD} , V_{CC} , R_{GEN} , R_i

Select V_{E_Q} ABOUT $2V_{DC}$ TO $3V_{DC}$

CASE 1; $R_{E1} + R_{E2}$ BOTH BYPASSED

CASE 2; $R_{E1} = R_{EF}$ NOT BYPASSED

$R_{E2} = R_{EB}$ BYPASSED

Find I_{LOAD}

$$I_{PEAK} = \frac{V_{OUT_PEAK}}{R_{LOAD}}$$

$$R_s = R_{GEN} + R_i$$

$$r_{\pi} = \frac{\beta v_t}{I_{CQ}}$$

CE AMP

2/5

Find I_{CQ} V_{CQ} R_C

Find V_{CQ}

20% V_{OUT} Do not
↓
DESIGN
FOR AN EDGE

$$V_{C_{MAX}} = V_{CC} - V_{OUT} - 0.2V_{OUT}$$

$$V_{C_{MIN}} = V_E + V_{CE_{SAT}} + V_{OUT} + 0.2V_{OUT}$$

$$V_{CE_{SAT}} \cong 0.2V$$

$$V_{CQ} = \frac{V_{C_{MAX}} - V_{C_{MIN}} + V_{C_{MIN}}}{2}$$

$$V_{CEQ} = V_{CQ} - V_{EQ}$$

Find I_{CQ} And R_C

$$V_{R_{CQ}} = V_{CC} - V_{CQ}$$

$$\Rightarrow I_{CQ} = V_{R_{CQ}} / R_C = \beta I_B$$

$$V_{OUT} = \beta I_B (R_E \parallel r_o \parallel R_L)$$

$$V_{OUT} = \beta I_B \frac{R_C (r_o \parallel R_L)}{R_C + (r_o \parallel R_L)} = \beta I_B \frac{V_{R_C} (r_o \parallel R_L)}{R_C + (r_o \parallel R_L)}$$

$$R_C = \frac{V_{R_C} (r_o \parallel R_L)}{V_{OUT} + 0.2V_{OUT}} - (r_o \parallel R_L)$$

CC Amp;
Find V_E, R_E, I_{CQ}

3/5

$$F_{ind} = \frac{V_E}{I_{CQ}}$$


$$V_{Emin} = V_{OUT} + 20\%V_{OUT}$$

$$V_{Emax} = V_{CC} - V_{CE(sat)} - V_{OUT} - 20\%V_{OUT}$$

$$V_{EQ} = \frac{V_{Emax} - V_{Emin}}{2} + V_{Emin}$$

Find R_E, I_{CQ}
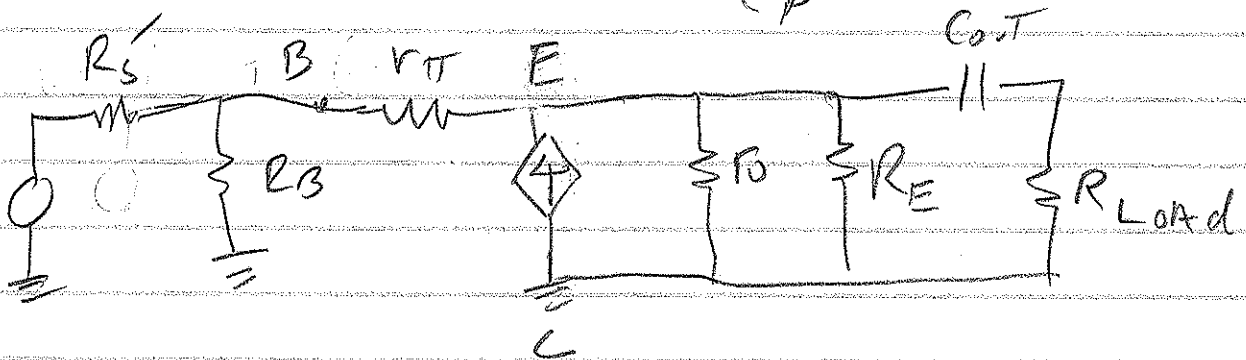
$$V_E = I_E R_E \quad I_E = \left(\frac{\beta + 1}{\beta} \right) I_C$$



$$V_{OUT} = I_E (R_E \parallel r_o \parallel R_L)$$

$$R_E = \frac{V_{RE} (r_o \parallel R_L)}{V_{OUT} - V_{OUT} + 20\%V_{OUT} (r_o \parallel R_L)}$$

$$I_E = \frac{V_{RE}}{R_E} = I_C = \frac{\beta}{\beta + 1} I_E$$

CC AMP Find r_o , 1
VE

4/5

$$R_E = \frac{I_E R_E (r_o \parallel R_L) - (r_o \parallel R_L)}{V_{oT} + 20\% V_{oT}}$$

$$R_E = \frac{V_{E_Q}}{V_{oT} + 0.2 V_{oT}} (r_o \parallel R_L) - (r_o \parallel R_L)$$

GUESS AT r_o

Find

r_o

From the curves find r_o , β
For CE use $I_C = (2.5) I_L$ To find r_o

CC use $I_C = (3.0) I_L$ To find r_o

AFTER you find a point \rightarrow check $r_o \rightarrow$ how close

$$I_{E_Q} = \frac{V_{E_Q}}{R_E} \quad I_{C_Q} = I_{E_Q} \frac{\beta}{\beta + 1}$$

CC

CS AMP CD AMP

5/5

For CS AMP Find R_D the same way you found R_C for CE AMP

And R_{SE} the same as R_E

For CD Find R_S the same way as you found R_E for CE AMP