

CE

1/9

Find R_{in} CE AMP Assume $r_o = \infty$
AT mid BAND

$$R_{in} = R_i + R_{in2}$$

$$R_B = R_{B1} \parallel R_{B2} = \frac{1}{\frac{1}{R_{B1}} + \frac{1}{R_{B2}}}$$


$$R_{in2} = R_B \parallel R_{inBASE}$$

R_{inBASE} = Impedance looking in
The BASE of TRANSISTOR

$$R_{inBASE} = r_{\pi} + R_{EF}(\beta + 1)$$

IF $R_{EF} = 0$ The $R_{inBASE} = r_{\pi}$
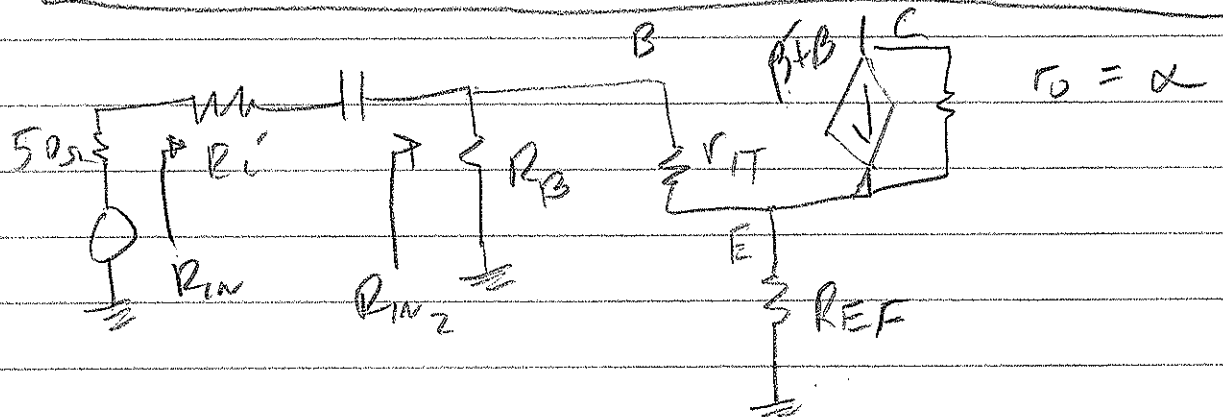
$$R_{in} = R_i + (R_{B1} \parallel R_{B2}) \parallel [r_{\pi} + R_{EF}(\beta + 1)]$$



R_{EF} is the non BYPASSED Emitter Resistor

CC

2/a

Find R_{in} CC AMP AT MIDBAND


$$R_{in} = R_i' + R_{in2}$$

$$R_B = R_{B1} \parallel R_{B2} = \frac{1}{\frac{1}{R_{B1}} + \frac{1}{R_{B2}}}$$

$$R_{in2} = R_B \parallel R_{in\text{BASE}}$$

$$R_{in\text{BASE}} = r_{\pi} + [R_E \parallel R_L \parallel R_o](\beta + 1)$$
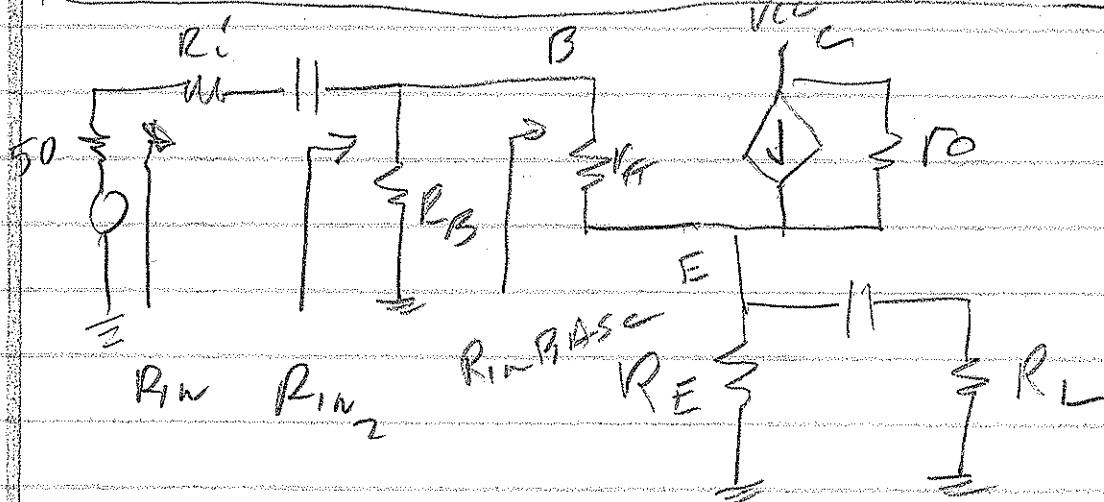
$$R_{in} = R_i' + (R_{B1} \parallel R_{B2}) \parallel [r_{\pi} + (R_E \parallel R_L \parallel R_o)(\beta + 1)]$$



CS

3/9

Find R_{in} CS AMP AT mid BAND


$$R_{in} = R_i' + R_{in2}$$

$$R_G = R_{G1} \parallel R_{G2} = \frac{1}{\frac{1}{R_{G1}} + \frac{1}{R_{G2}}}$$

$$R_{in2} = R_G \parallel R_{in \text{ Gate}}$$

$$R_{in \text{ Gate}} = \infty$$
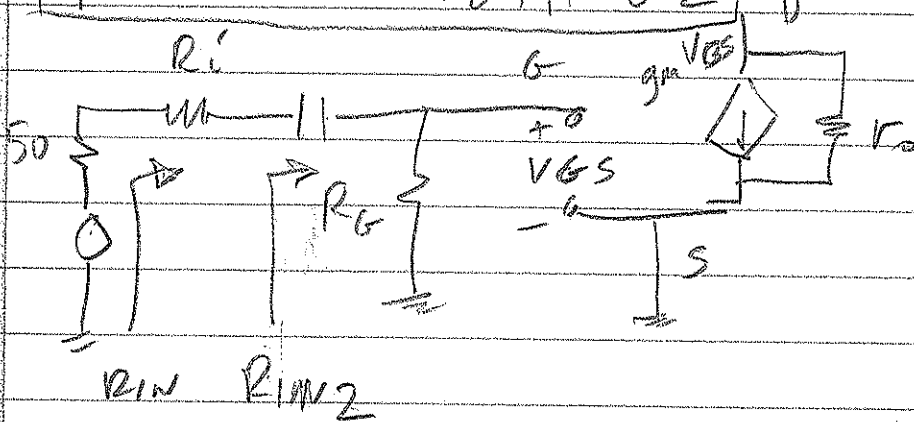
$$R_{in} = R_i' + R_{G1} \parallel R_{G2}$$



CD

4/9

Find R_{in} CD amp AT mid BAND


$$R_{in} = R_i + R_{in2}$$

$$R_G = R_{G1} \parallel R_{G2} = \frac{1}{\frac{1}{R_{G1}} + \frac{1}{R_{G2}}}$$

$$R_{in2} = R_G \parallel R_{inGate}$$

$$R_{inGate} = \alpha$$
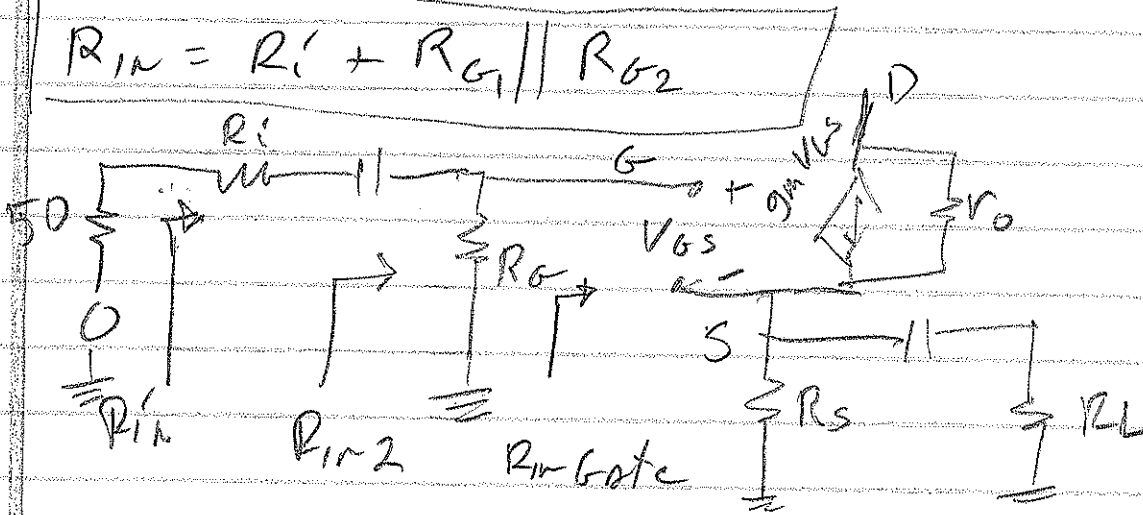
$$R_{in} = R_i + R_{G1} \parallel R_{G2}$$



CE CC

5/9

Find R_{B1} , R_{B2} To MEET
 R_{in} REQUIREMENT.

$$R_{in} = R_i + R_{in2} \quad \text{GIVE } R_{in}$$

$$R_{in2} = R_{in} - R_i \quad \text{SET}$$

$$R_{in2} = R_B \parallel R_{inBASE}$$

R_{inBASE} IS SET BY THE BIAS /
Q-POINT.

$$CE \quad R_{inBASE} = V_{T1} + R_{EF}(\beta + 1)$$

$$CC \quad R_{inBASE} = V_{T1} + (R_{E} \parallel R_L \parallel r_o)(\beta + 1)$$

$$R_{in2} = R_B \parallel R_{inBASE} = \frac{1}{\frac{1}{R_B} + \frac{1}{R_{inBASE}}}$$

SOLVE FOR R_B

$$\frac{1}{R_B} = \frac{1}{R_{in2}} - \frac{1}{R_{inBASE}}$$

$$R_B = \frac{1}{\frac{1}{R_{in2}} - \frac{1}{R_{inBASE}}}$$

CE CC

6/9

Given $R_{in} = \text{value}$ Solve for R_{B1} and R_{B2} from R_B

$$R_B = \frac{1}{\frac{1}{R_{B1}} + \frac{1}{R_{B2}}}$$

Now solve for R_{B2}

$$\frac{1}{R_{B2}} = \frac{1}{R_B} - \frac{1}{R_{B1}}$$

Write R_{B1} in terms of R_{B2}

$$R_{B1} = \frac{V_{CC} - V_b}{\frac{V_b}{R_{B2}} + I_B}$$

Substitute in R_{B1}

$$\frac{1}{R_{B2}} = \frac{1}{R_B} - \frac{1}{\frac{V_{CC} - V_b}{\frac{V_b}{R_{B2}} + I_B}}$$

Give $R_{in} = \text{value}$ CECC $\frac{7}{9}$

Find R_{B1} , R_{B2} cont.

Reduce:

$$\frac{1}{R_{B2}} = \frac{1}{R_B} - \left(\frac{V_B / R_{B2} + I_B}{V_{CC} - V_B} \right)$$

Multiply by $V_{CC} - V_B$

$$\frac{V_{CC} - V_B}{R_{B2}} = \frac{V_{CC} - V_B}{R_B} - \left(\frac{V_B + I_B R_{B2}}{R_{B2}} \right)$$

Re arrange

$$\frac{V_B}{R_{B2}} + I_B + \frac{V_{CC} - V_B}{R_{B2}} = \frac{V_{CC} - V_B}{R_B}$$

$$\frac{V_{CC}}{R_{B2}} + I_B = \frac{V_{CC} - V_B}{R_B}$$

$$\frac{V_{CC}}{R_{B2}} = \frac{V_{CC} - V_B}{R_B} - I_B$$

$$R_{B2} = V_{CC} / \left(\frac{V_{CC} - V_B}{R_B} - I_B \right)$$

$$R_{B1} = \frac{V_{CC} - V_B}{\frac{V_B}{R_{B2}} + I_B}$$

Given $R_{IN} = \text{Value}$ CS CD ^{B/q}

Find R_{G1} and R_{G2}

$$R_{IN} = R_i + R_{IN2} \Rightarrow R_{IN2} = R_{IN} - R_i$$

$$R_{IN2} = R_{G1} \parallel R_{G2} \parallel R_{IN \text{ Gate}}$$

$$R_G = R_{G1} \parallel R_{G2} = \frac{1}{\frac{1}{R_{G1}} + \frac{1}{R_{G2}}}$$

$$R_{IN \text{ Gate}} = \alpha$$

$$R_{IN2} = R_G$$

$$\frac{1}{R_G} = \frac{1}{R_{G1}} + \frac{1}{R_{G2}}$$

Solve R_{G2}

$$\frac{1}{R_{G2}} = \frac{1}{R_G} - \frac{1}{R_{G1}}$$

$$R_{G1} = \frac{V_{DD} - V_G}{\frac{V_G}{R_{G2}}}$$

$$I_{R_{G1}} = I_{R_{G2}}$$

$R_{G1} = \frac{\text{Voltage across}}{\text{Current in } R_{G1}}$

CS, CD

9/9

$$\frac{1}{R_{G2}} = \frac{1}{R_G} - \frac{1}{\frac{V_{DD} - V_G}{\frac{V_G}{R_{G2}}}}$$

$$\frac{1}{R_{G2}} = \frac{1}{R_G} - \frac{V_G / R_{G2}}{V_{DD} - V_G}$$

$$\frac{V_{DD} - V_G}{R_{G2}} = \frac{V_{DD} - V_G}{R_G} - \frac{V_G}{R_{G2}}$$

$$\frac{V_{DD} - V_G}{R_{G2}} + \frac{V_G}{R_{G2}} = \frac{V_{DD} - V_G}{R_G}$$

$$\frac{V_{DD}}{R_{G2}} = \frac{V_{DD} - V_G}{R_G} \Rightarrow R_{G2} = \frac{R_G}{\frac{V_{DD} - V_G}{V_{DD}}}$$

$$R_{G2} = \frac{R_G V_{DD}}{V_{DD} - V_G}$$

$$R_{G1} = \frac{V_{DD} - V_G}{V_G / R_{G2}}$$

$$R_{IN2} = R_G$$
$$R_{IN} = R_i + R_{IN2}$$